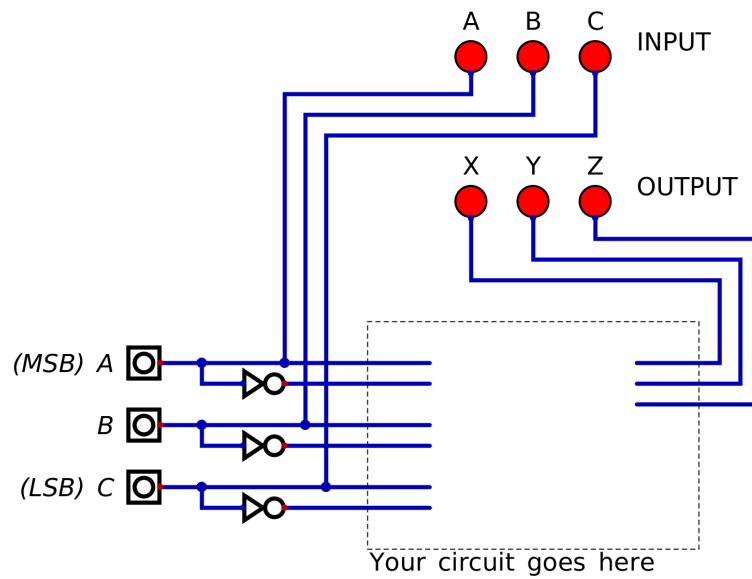


Using the template provided in *template.dig*



design and demonstrate a 3-bit Gray code to digital converter. (Erase the text box, if needed.)

A	B	C	X	Y	Z
0	0	0	0	0	0
0	0	1	0	0	1
0	1	0	0	1	1
0	1	1	0	1	0
1	0	0	1	1	1
1	0	1	1	1	0
1	1	0	1	0	0
1	1	1	1	0	1

Upload *template.dig* to SUcourse at the end of the session.

□